

2024

BCA

BCA First Semester End Examination - 2024

PAPER - CC102P

Full Marks : 30

Time : 2 hours

*The figures in the right-hand margin indicate marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

*Illustrate the answers wherever necessary.*

Answer any one question :

20×1=20

1. Design a full adder using NAND gates and verify the truth table.
2. Implement  $Y = (X+Z).(\bar{X}+Y)$  using basic gates and verify its truth table.
3. Design gray code to BCD code converter and verify the truth table.
4. Design SR F/F using NAND gates.
5. Simplify the following function using K-map and implement using basic gates.  $A = \sum m(0, 5, 7, 13, 14, 15)$

(Turn Over)

6. Design a half adder using NOR gates and verify the truth table.
7. Design a circuit to convert BCD code to Excess-3 code.
8. Design J-K master-slave F/F and verify the truth table
9. Design a 4:1 MUX using NOR gates and verify the truth table.
10. Implement  $F = (\bar{A}B + A)(B + A\bar{C})$  using basic gates and verify its truth table.
11. Design a 4 bit shift register using flip flops.
14. Implement  $w = \overline{xy} + x + \overline{y} + z$  using only NAND gates and verify the truth table.
13. Implement OR, NOR and X-OR gates using NAND gates and verify the truth table.
14. Implementation of 4-Bit Parallel Adder using 4783 IC.
15. Simplify the following function using K-map and implement using NAND gates.  $Y(A,B,C) = \Sigma(0,2,4,5,6)$
16. Design a 2:4 decoder using NAND gates and verify the truth table.
17. Design and implement the logic circuit for half-subtractor. Then verify the truth table.

18. Design and implement the logic circuit for 4:1 MUX using gates. Then verify the truth table.
19. Design and implement the logic circuit for S-R flip flop using NOR/NAND gates. Then verify the truth table.
20. Design and implement the logic circuit for J-K flip flop using NOR/NAND gates. Then verify the truth table.

VIVA - 06

PNB - 04